
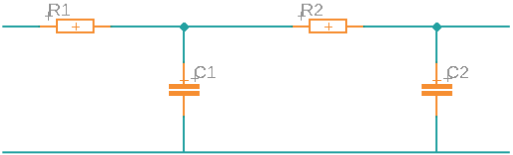


Introduction to Active Filters

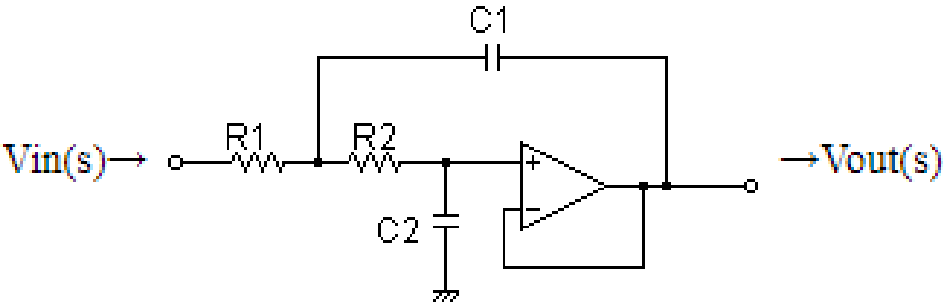


Too much attenuation at the cut-off frequency!

Much better approach is the use of active filters in e.g. sallen key topology:



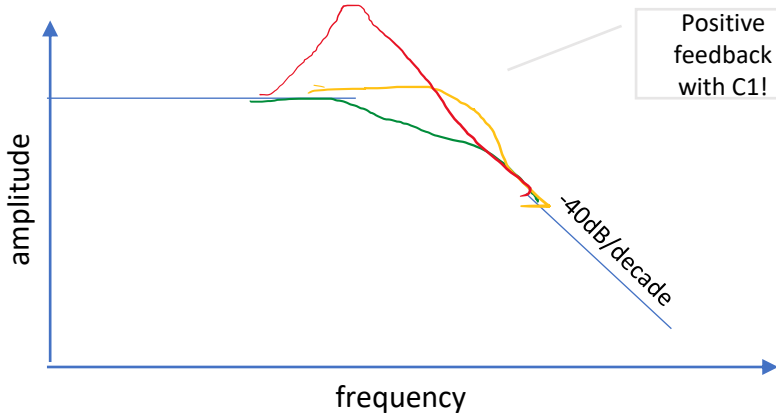Low frequencies: C1 and C2 open: → buffer amp
 High frequencies: C1 and C2 short: → R1C1 and R2C2 in series




green: C1 = C2
 yellow: C1 > C2
 red: C1 >> C2
 (different Qs)

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2}$$

Adding different stages with different Qs together allows to design Butterworth, Bessel or Chebyshev filters.

Most common topologies (lowpass):

Sallen Key

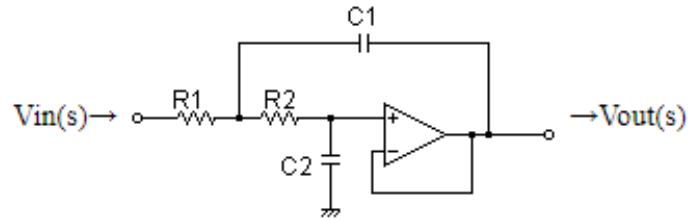


Transfer function:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{s^2 + s \left(\frac{1}{R_2 C_1} + \frac{1}{R_1 C_1} \right) + \frac{1}{R_1 C_1 R_2 C_2}}$$

- less components
- non-inverting
- noise gain = 1 @stage gain 1
- magnitude increase at higher frequencies
- better for low-/highpass -filter

Multiple Feedback

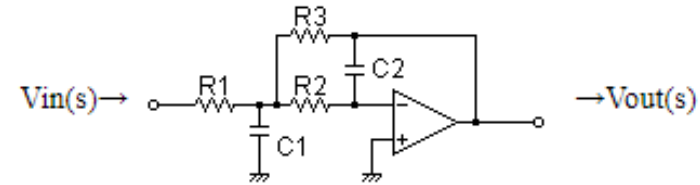


Transfer function:

$$\frac{v_o}{v_i} = \frac{-1}{s^2 + s \frac{1}{C_1} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) + \frac{1}{C_1 C_2 R_2 R_3}}$$

- more components
- inverting
- noise gain 1+1 = 2
- better for high Q, high gain -> lower magnitude envelope increase
- better for bandpass filters (high Q needed)

Active Filters (Sallen Key)

Second Order Low Pass Filter

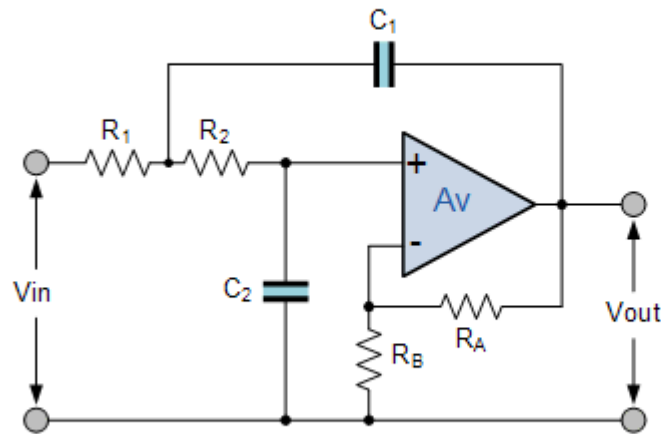

Gain (A_v) = $1 + \frac{R_A}{R_B}$


If Resistor and Capacitor values are different:
 $f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$

If Resistor and Capacitor values are the same:
 $f_c = \frac{1}{2\pi RC}$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2}$$

Q is a measure of the peaking of a filter

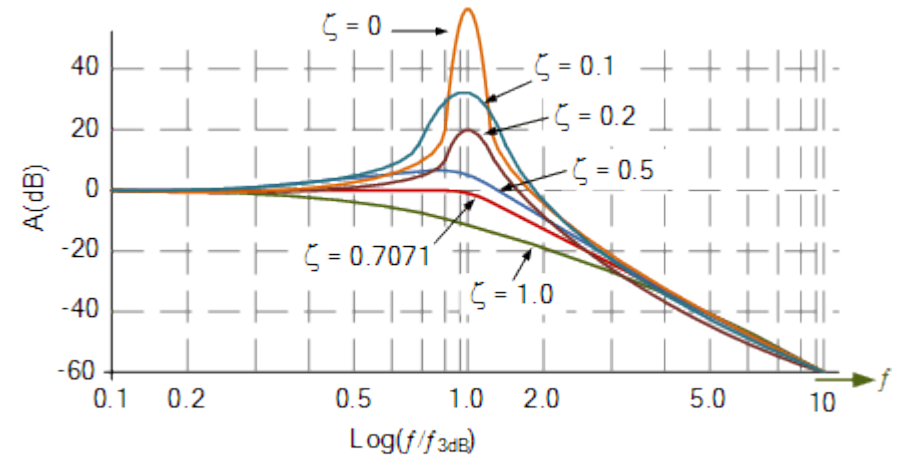Damping factor (zeta) = $\zeta = \frac{1}{2Q}$



- undamped ($\zeta = 0$)
- underdamped ($\zeta < 1$)
- critically damped ($\zeta = 1$)
- overdamped ($\zeta > 1$).



Q of 2 means, peak is aprox. 2x amplitude at f_c

Active Filters



Lowpass Filter-2nd order Butterworth

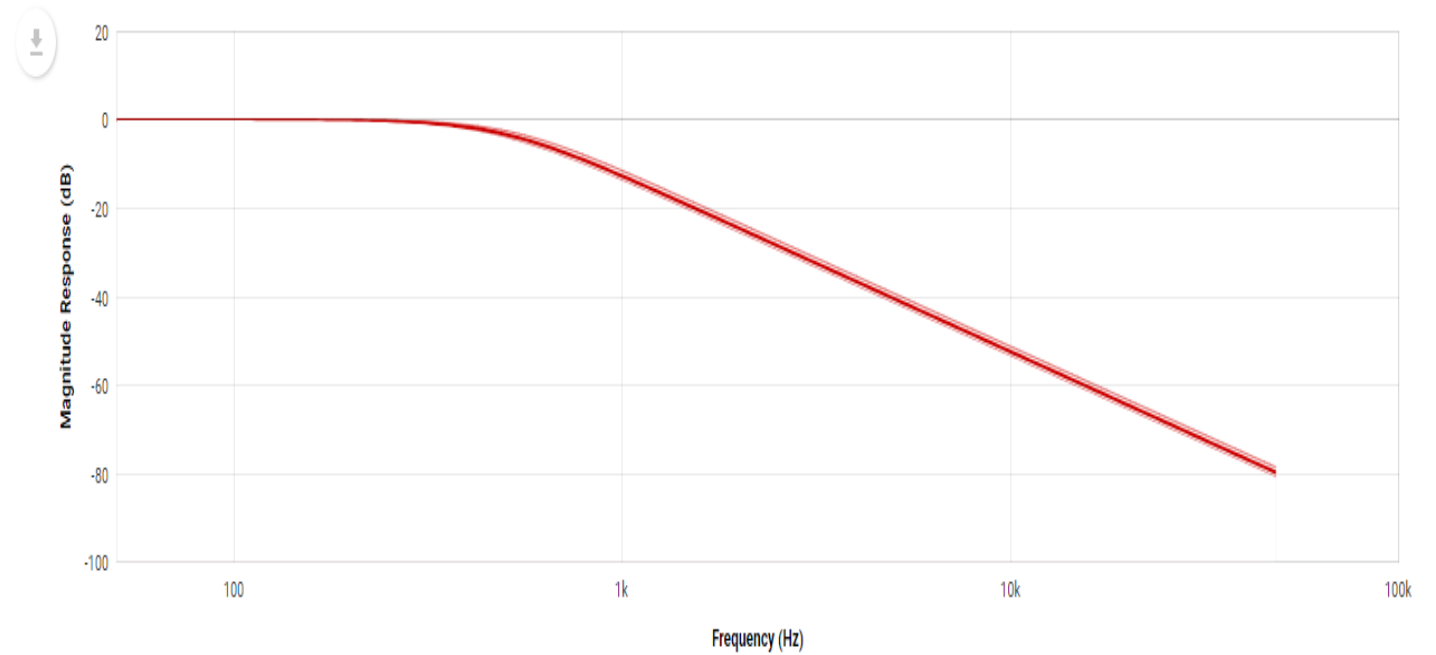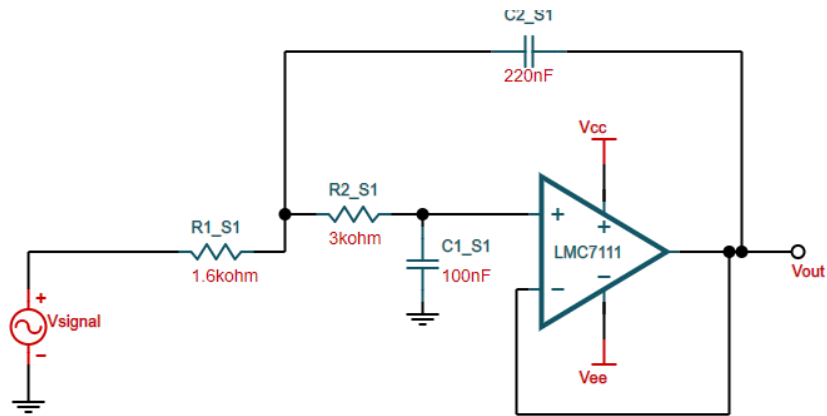Passband: A_o : 1.000 V/V, F_p : 500 Hz, R_p : 1.000 dB Stopband: F_s : 5 kHz, A_{sb} : -40.00 dB



<https://www.youtube.com/watch?v=llilxWXCj1g>

Active Filters

Bench tests

...

Active Filters