



# Crystal-Ladder-Filter design

Crystal-Ladder-Filter have...




- very high Q
- very narrow band

However, they...

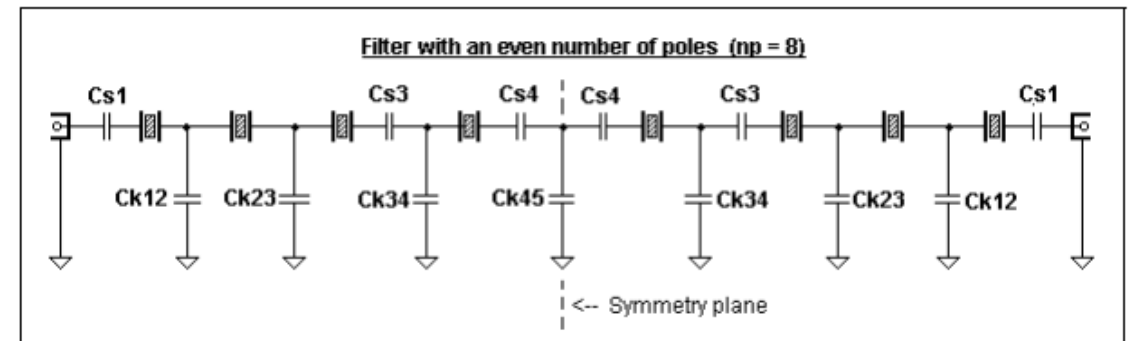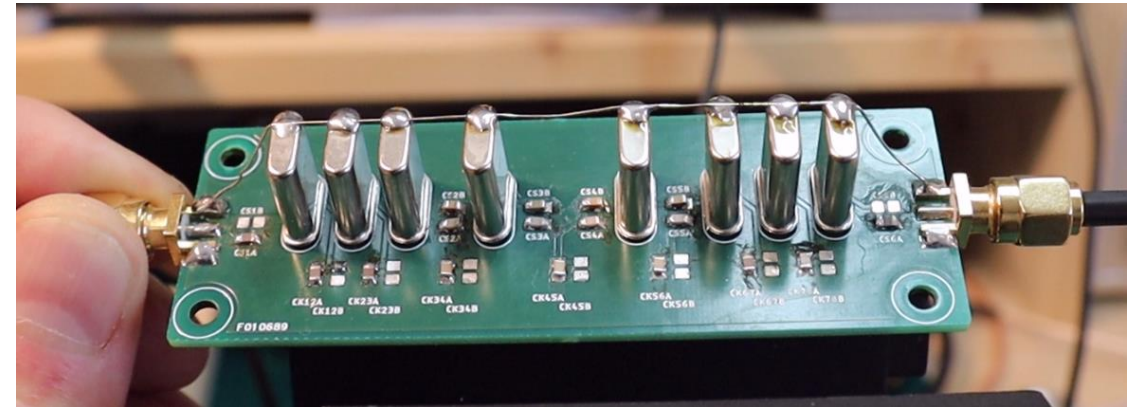
- good only for a few kHz bandwidth
- only bandpass or bandstop
- not 50Ω
- crystal true replacement values (characteristics) are unknown
- need to select crystals



# Characterizing Xtal

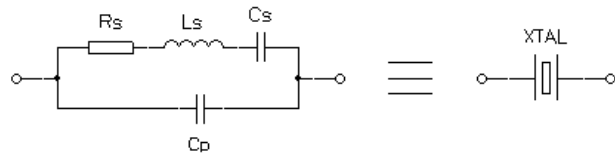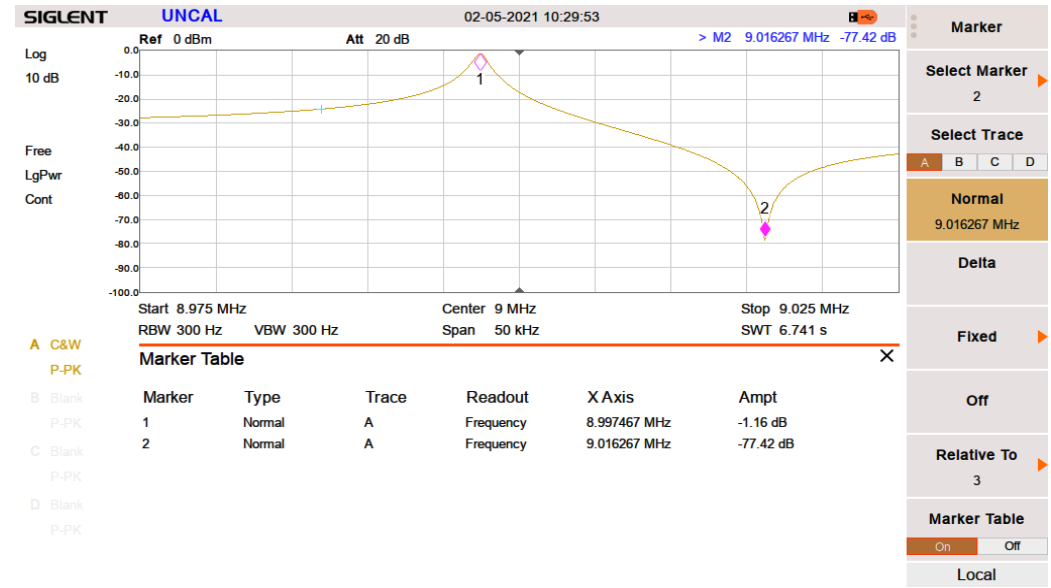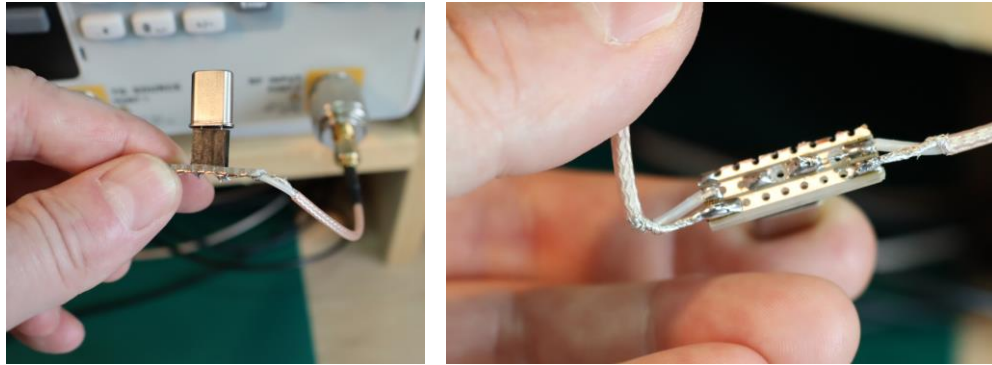

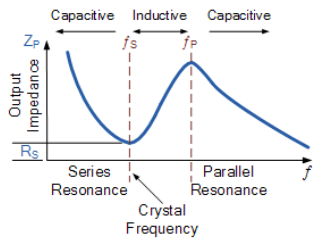Cs: motional capacitance  
 Ls: motional inductance  
 Rs: series loss resistance  
 Rp: "holder" capacitance




$$R = R \quad \text{and} \quad X_{Ls} = 2\pi f L_s$$

$$X_{Cs} = \frac{1}{2\pi f C_s} \quad \text{and} \quad X_{Cp} = \frac{1}{2\pi f C_p}$$

$$Z_s = \sqrt{R_s^2 + (X_{Ls} - X_{Cs})^2}$$

$$\therefore Z_p = \frac{Z_s \times X_{Cp}}{Z_s + X_{Cp}}$$

Cp measured with LCR meter: 5.3pF

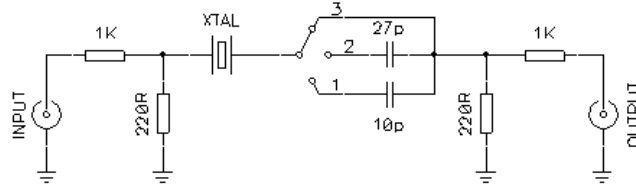

Crystal parallel resonance frequency:  $f_p = 9.016253$  MHz

Crystal series resonance frequency (10 pF):  $f_{s1} = 9.002827$  MHz

Crystal series resonance frequency (27 pF):  $f_{s2} = 9.000093$  MHz

Crystal series resonance frequency (no capacitor):  $f_{s3} = 8.997387$  MHz

Actual (measured) C1 capacitance:  $C_1 = 10$  pF

Actual (measured) C2 capacitance:  $C_2 = 27$  pF



Crystal series capacitance:  $C_s = 20.347$  fF

Crystal series inductance:  $L_s = 15.379$  mH


Crystal parallel capacitance:  $C_p = 4.852$  pF

<https://www.giangrandi.org/electronics/crystalfilters/xtaltest.html>
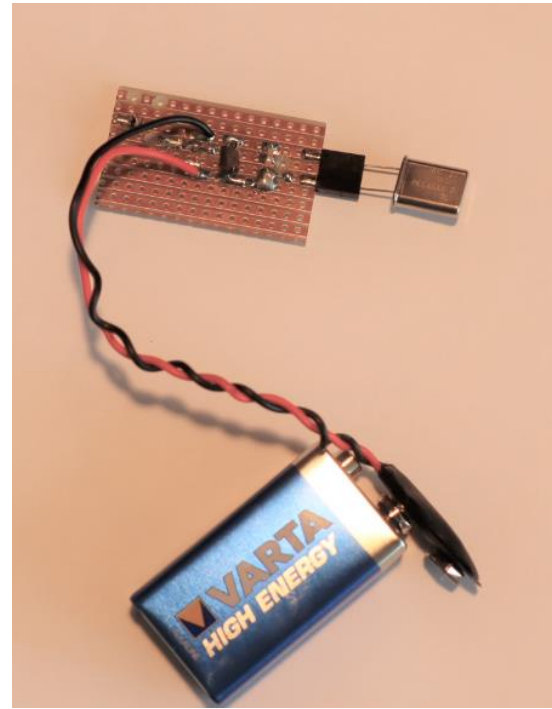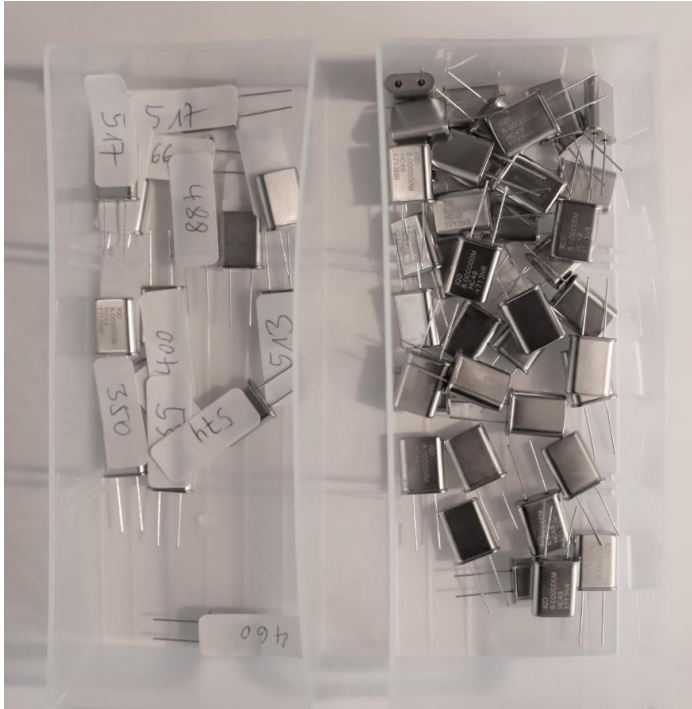
# Selecting matching crystals to +/- 50 Hz





colpitts oscillator with 2N3904

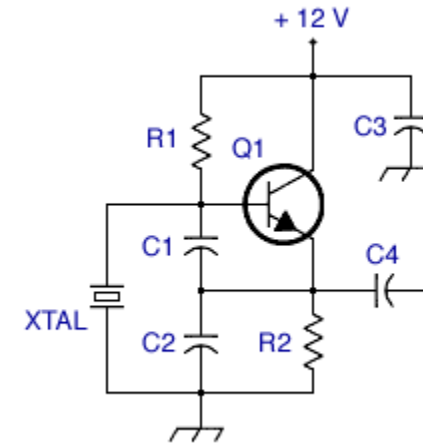

- C1: 100 pF ceramic disc or silver mica
- C2: 680 pF ceramic disc or silver mica
- C3: .01 uF ceramic disc
- C4: .001 uF ceramic disc
- Q1: 2N3904
- R1: 220 K
- R2: 1 K

To the bench...

# Dishal filter calculator and results

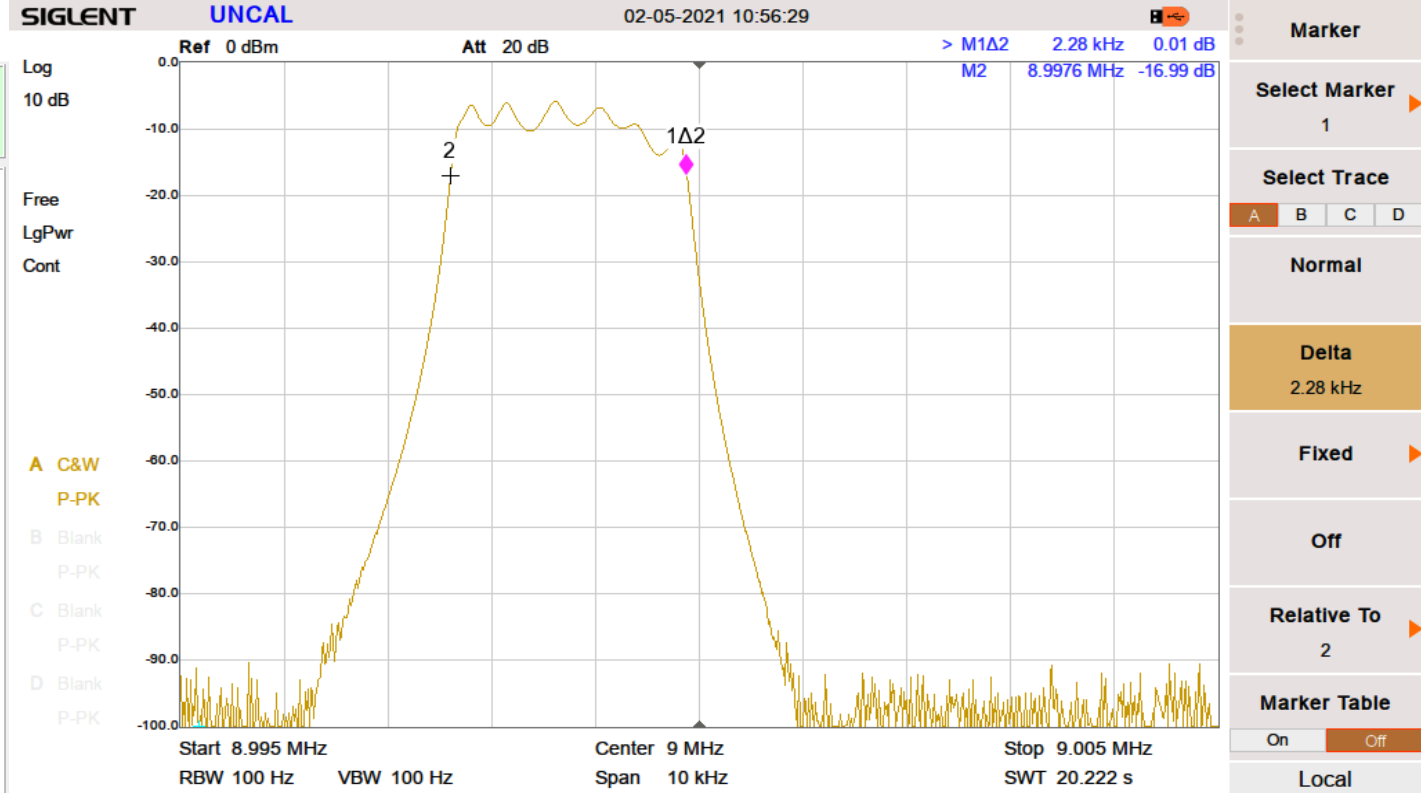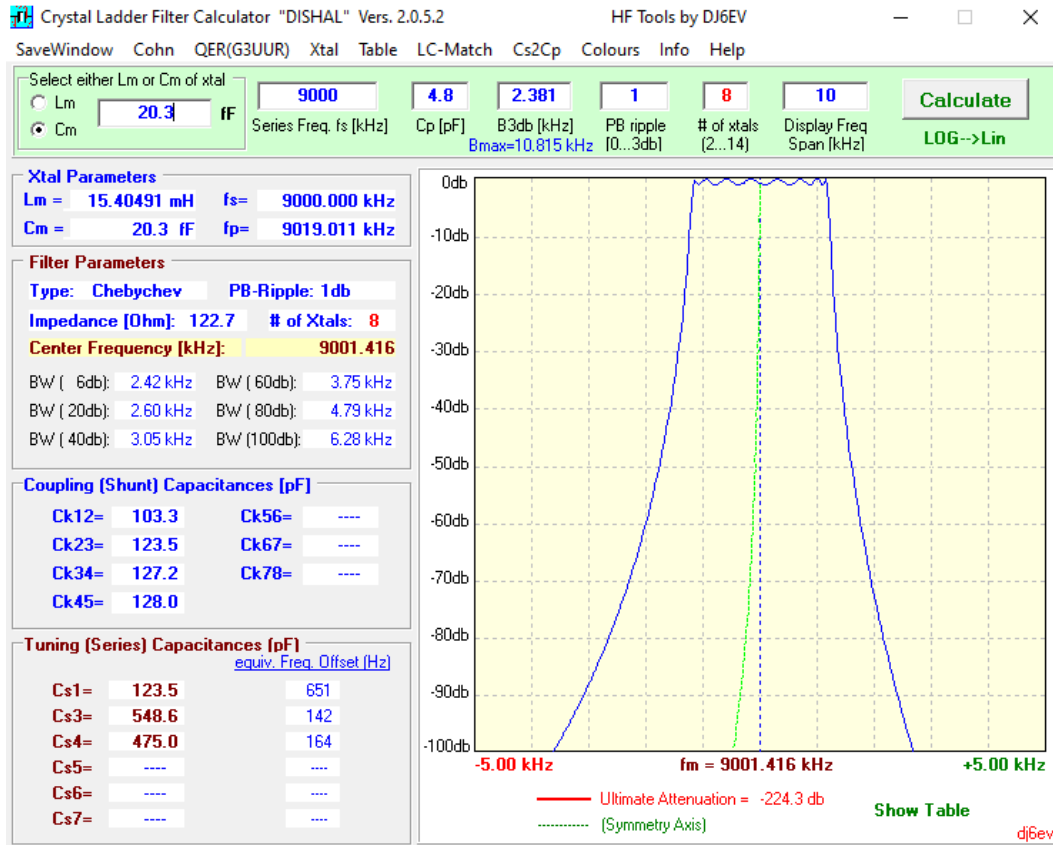

- additional tuning needed
- impedance matching