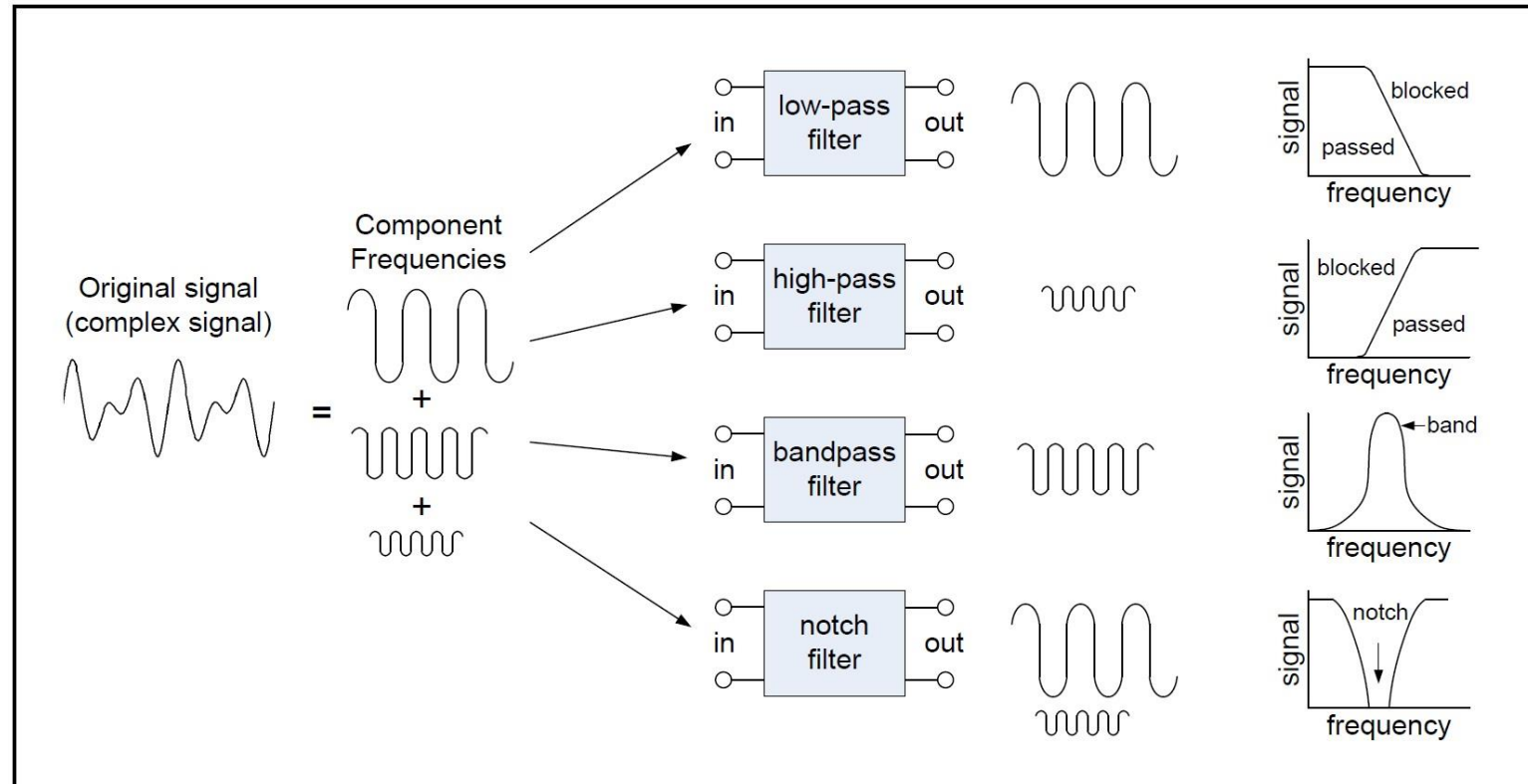


Introduction to electronic filters – some theory and practical experiments

1. Introduction to electronic filters
2. [Analog Filters](#)
3. [Crystal Filters](#)
4. Active Filters
5. Digital Filters
6. FFT basics

Introduction

A filter is a circuit capable of passing (or amplifying) certain frequencies while attenuating other frequencies. Thus, a filter can extract important frequencies from signals that also contain undesirable or irrelevant frequencies.




Key terms

Response curve (V_{out} / V_{in}) with attenuation in dB

f_c, f_1, f_2 = corner frequency (in Hz or ω); f_{3dB} = minus 3 dB frequency = cutoff frequency = half-power frequency = $V_{out} = \frac{V_{in}}{\sqrt{2}}$

f_s = stop band frequency (defined attenuation has been reached)

B.W. = bandwidth or β

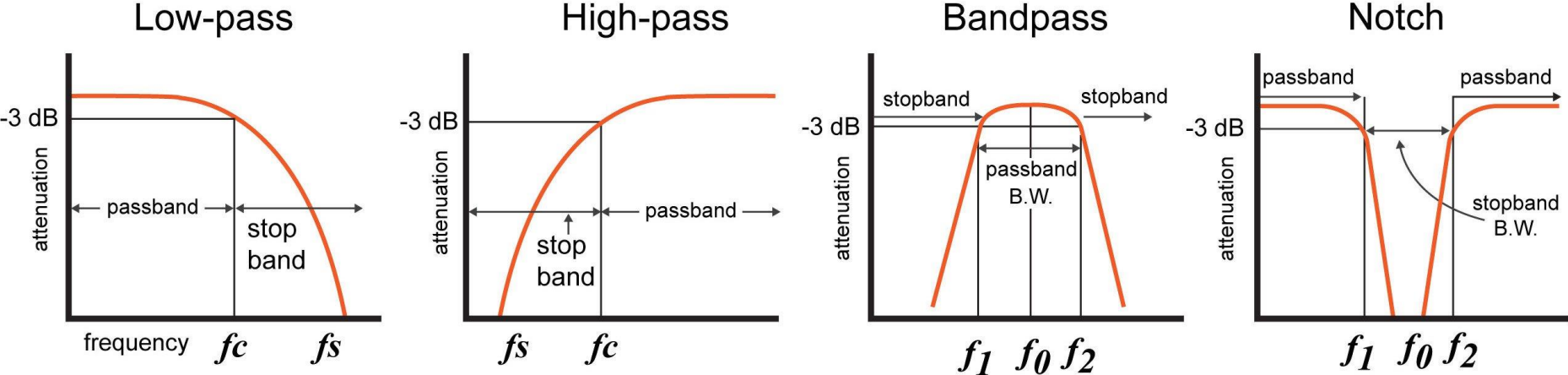

RC Lowpass

Simplest, 1st order low pass filter.


$$V_{out} = V_{in} * \frac{Z_2}{Z_1 + Z_2}$$

$$Z_2 \rightarrow C_1 \rightarrow X_c = \frac{1}{2\pi f C_1}$$

$$V_{out} = V_{in} * \frac{Z_2}{Z}$$

$$Z = \sqrt{R_1^2 + X_c^2}$$

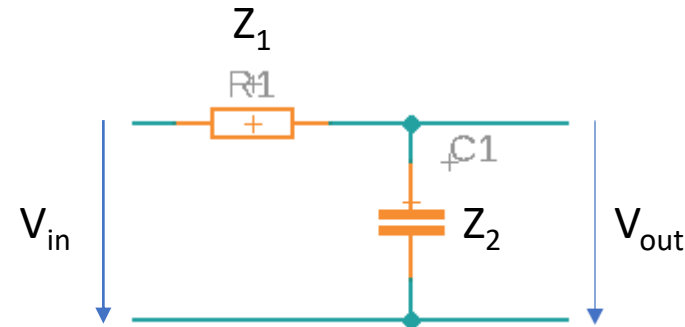$V_{in} = 10V$
 $R1 = 4.7k\Omega$
 $C1 = 47nF$
 $f_c = \frac{1}{2\pi R_1 C_1} = 720Hz$
 $f = 100Hz: V_{out} = 9.9V$
 $f = 10kHz: V_{out} = 0.72V$



Voltage transfer function: $H(\omega) = \frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} \quad \rightarrow \quad H_{RC}(\omega) = \frac{1}{1 + j\omega RC}$

Cut-off frequency def. = $|H_{RC}(\omega)| = \frac{1}{\sqrt{2}} = \mathbf{0.707} \quad \rightarrow \quad j\omega RC = 1 \quad \rightarrow \quad f_c = \frac{1}{2\pi RC}$

Phase at cut-off: $H_{RC}(\omega) = 1/(1+j\frac{1}{RC} RC) \quad \rightarrow \quad \cos(1) = 45^\circ$

```
octave:1> 1/(1+j)
ans = 0.5000 - 0.5000i
```



1st order RC lowpass

-20db/decade = -6dB/octave

Octave: 1 octave is the ratio of 2 of a frequency


Decade: 1 decade is the ratio of 10 of frequency

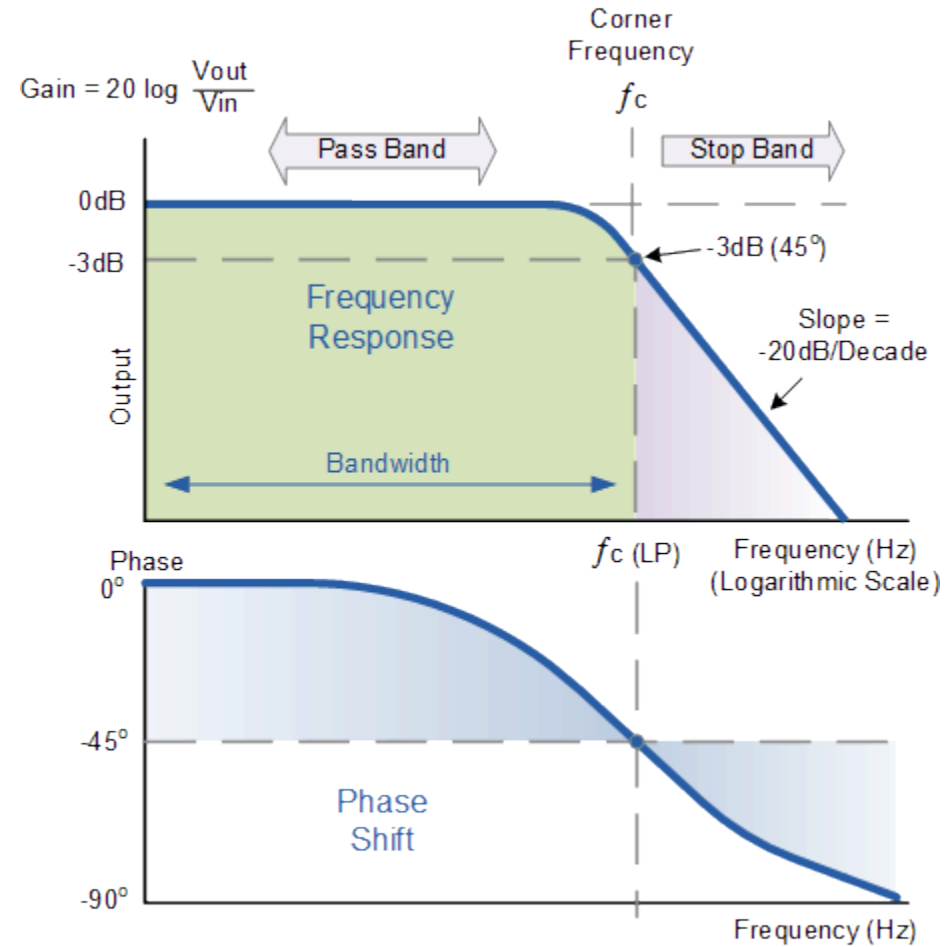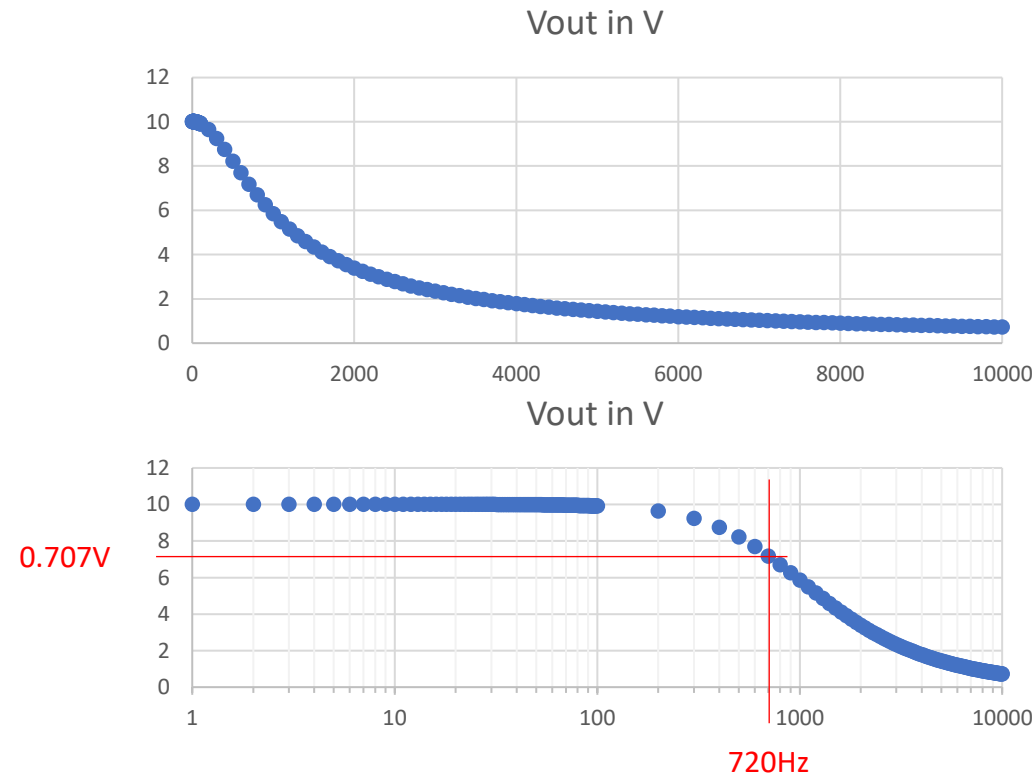An octave is 3.332 times in a decade ($2^x = 10$)



To the bench...

Lowpass “higher orders”

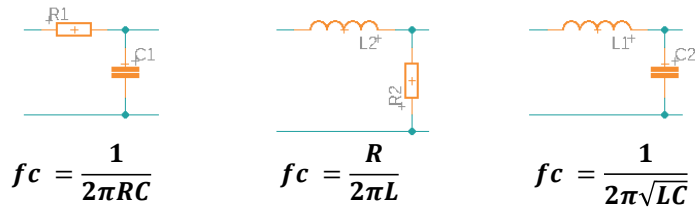

$$f_c = \frac{1}{2\pi RC}$$


$$f_c = \frac{R}{2\pi L}$$

$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

1st order

2nd order

X

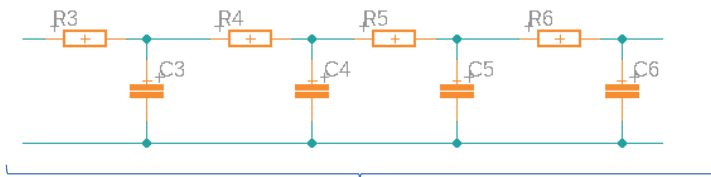


4th order

Higher the order (or poles) of a filter -> faster rolloff rate


Filter order -> derived from transfer function

Filter order -> minimum number of reactive components requir

Butterworth Response

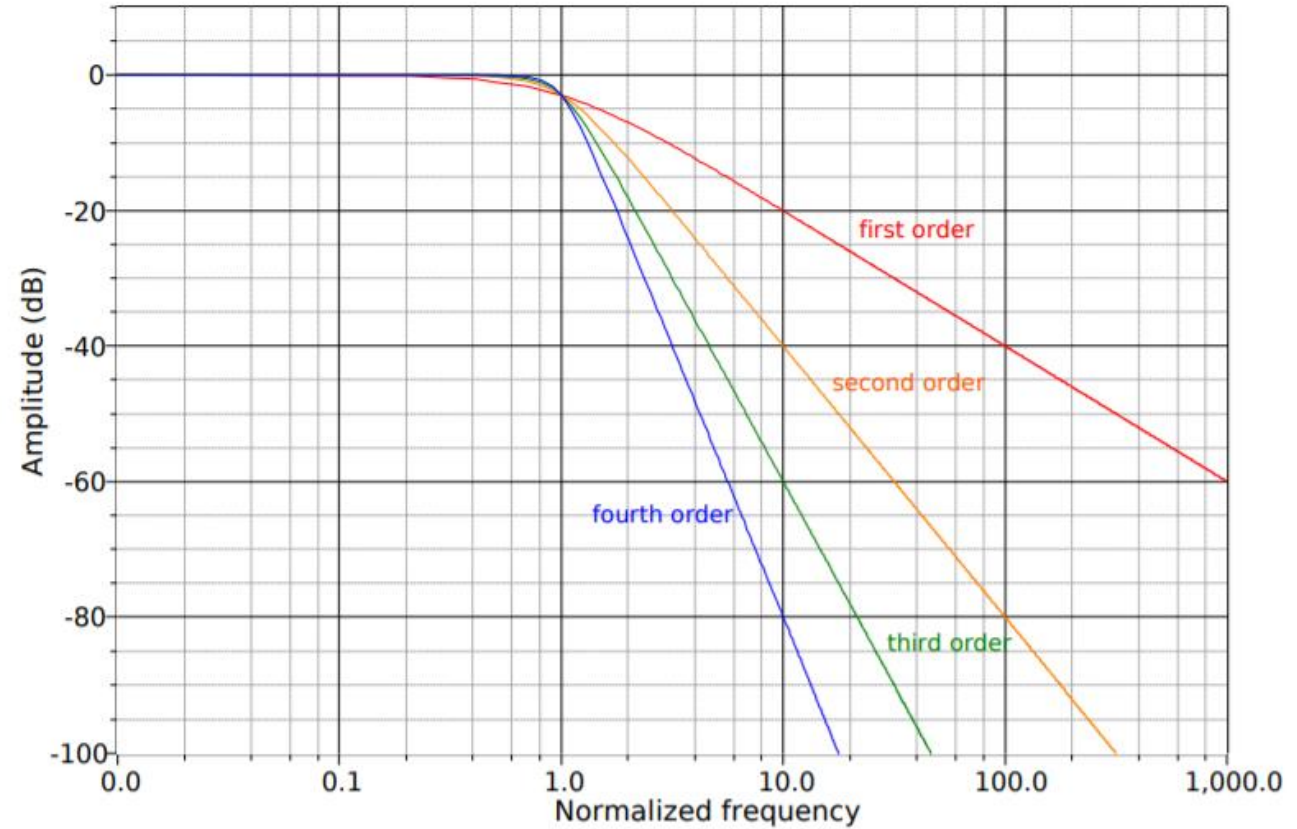

2nd order RC lowpass

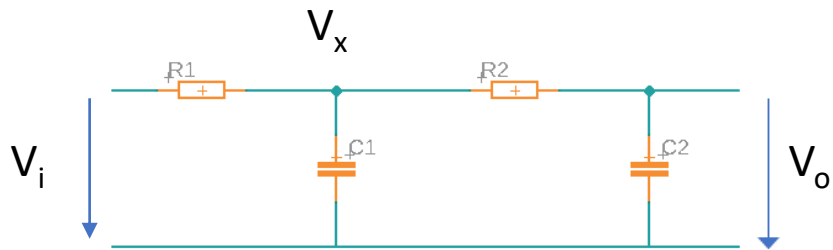

$$f_n = \frac{1}{(2\pi * \sqrt{R_1 R_2 C_1 C_2})}$$

= natural frequency (resonance) not
-3dB cutoff frequency!

I: KCL in V_o :

$$\frac{V_o - V_x}{R_2} + sC_2 V_o = 0$$

$$V_x = V_o(1 + sR_2 C_2)$$

II: KCL in V_x :



$$\frac{V_x - V_i}{R_1} + \frac{V_x - V_o}{R_2} + sC_1 V_x = 0$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 R_1 R_2 C_1 C_2 + s(R_1 C_1 + R_1 C_2 + R_2 C_2) + 1}$$

Take aways:

- Loading of second stage changes reduces cut-off freq.
- Loading of the output affects the filter behavior as well!

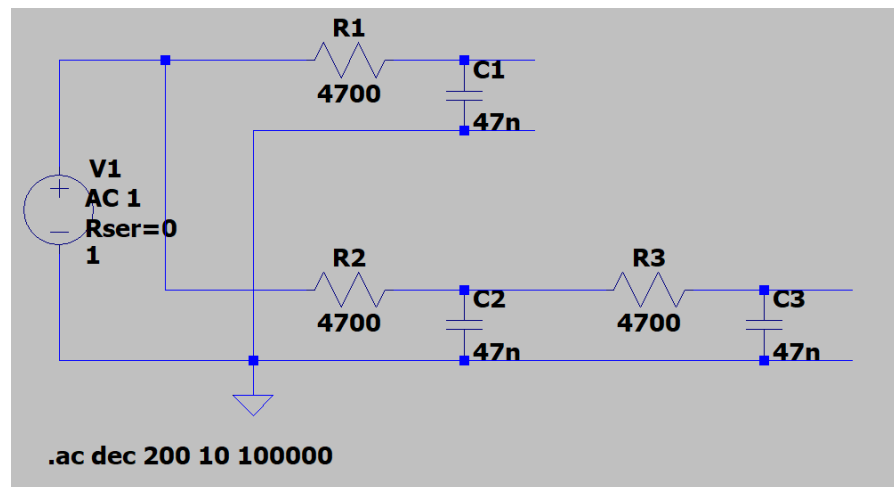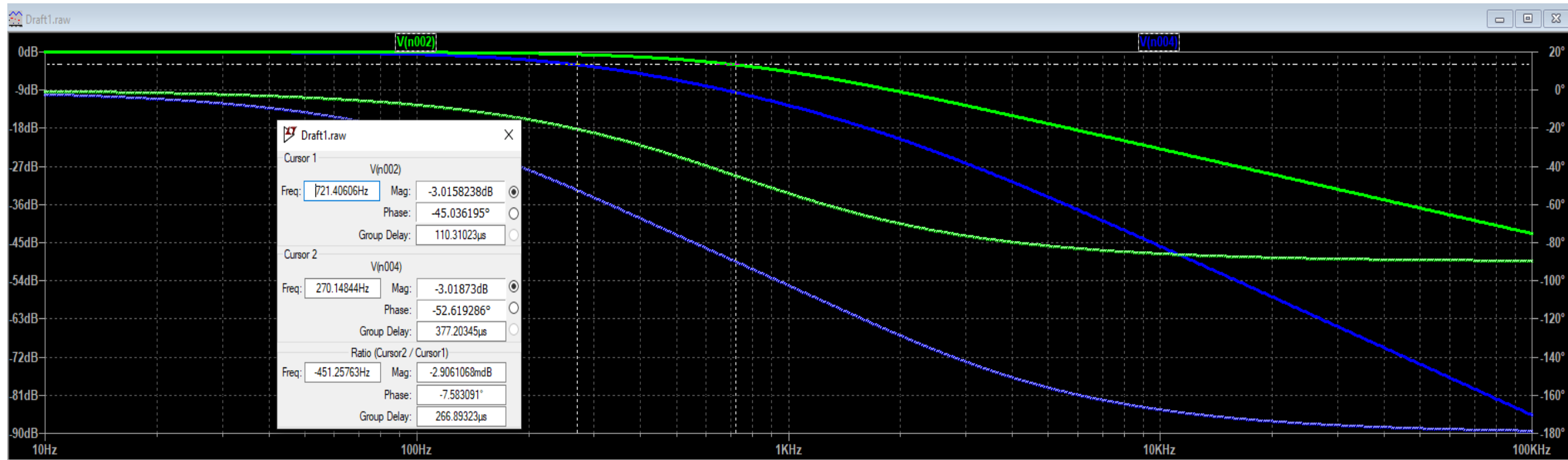
1st vs. 2nd order lowpass filter simulated




$$f_n = \frac{1}{(2\pi * \sqrt{R_1 R_2 C_1 C_2})}$$

$f_n = 720\text{Hz}$
 $f_c = 270\text{Hz}!!$

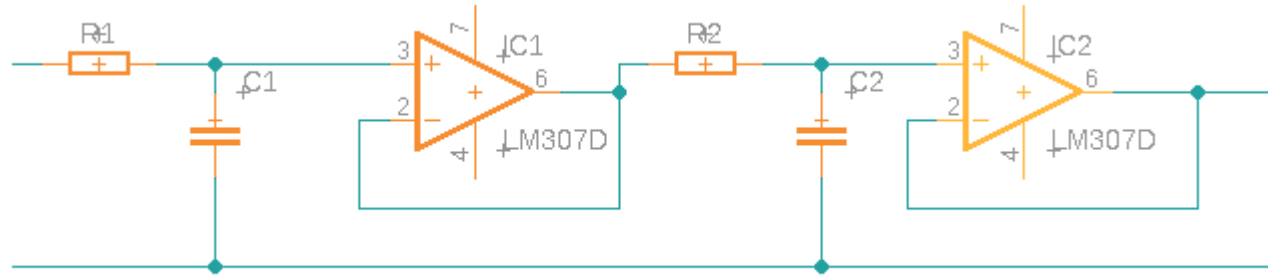RC lowpass 2nd order; decoupling the outputs



Second Order Low Pass Filter

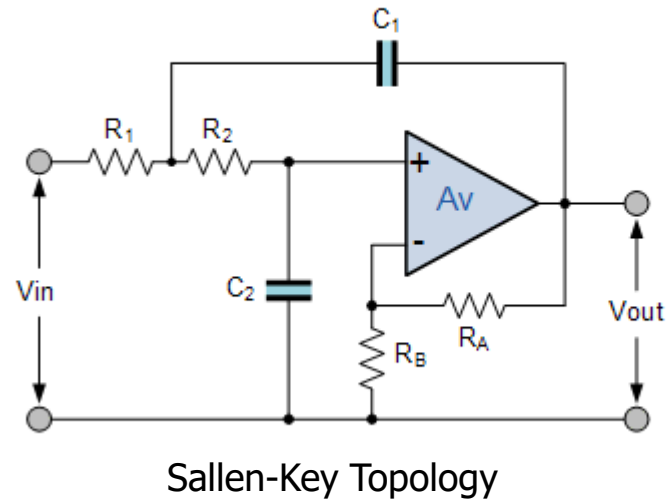

$$\text{Gain } (A_v) = 1 + \frac{R_A}{R_B}$$

If Resistor and Capacitor values are different:

$$f_c = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$



If Resistor and Capacitor values are the same:

$$f_c = \frac{1}{2\pi RC}$$

To the bench...

Filter types

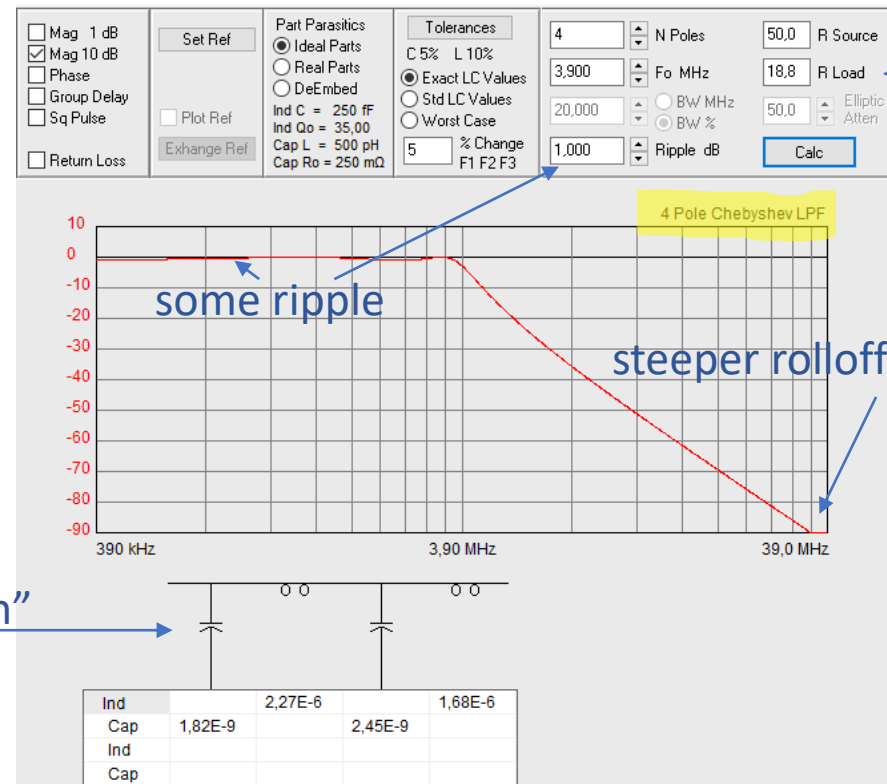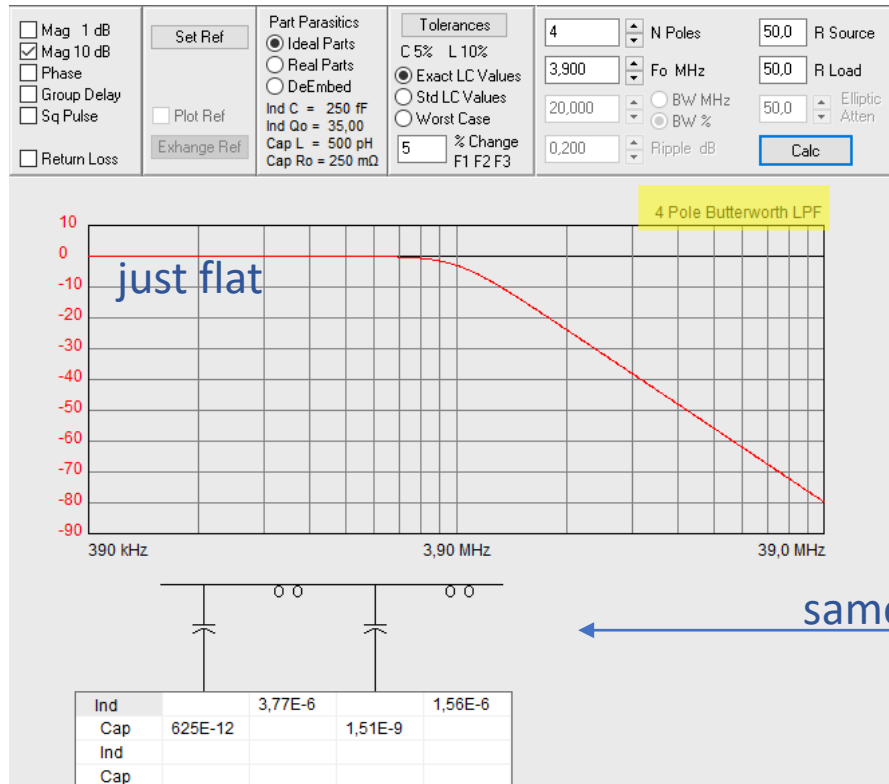From “Iowa Hills RF Filter Designer Version 2.2”, we find for a lowpass, $f_c = 3.9\text{MHz}$, 50Ω , the following answers:



lower output impedance

same “design”


Using different coefficients for the calculation of the filter, forces the same filter “design” to perform electrically different.

used here: <http://www.iowahills.com/8DownloadPage.html>


nice online tool: <https://rf-tools.com/lc-filter/>

Typical Filter Characteristics

	Advantages	Disadvantages
Butterworth	flat in passband	ringing in step response
Chebyshev	better attenuation pass band	ripple in passband ringing in step response
Bessel	excellent step response	passband not so flat

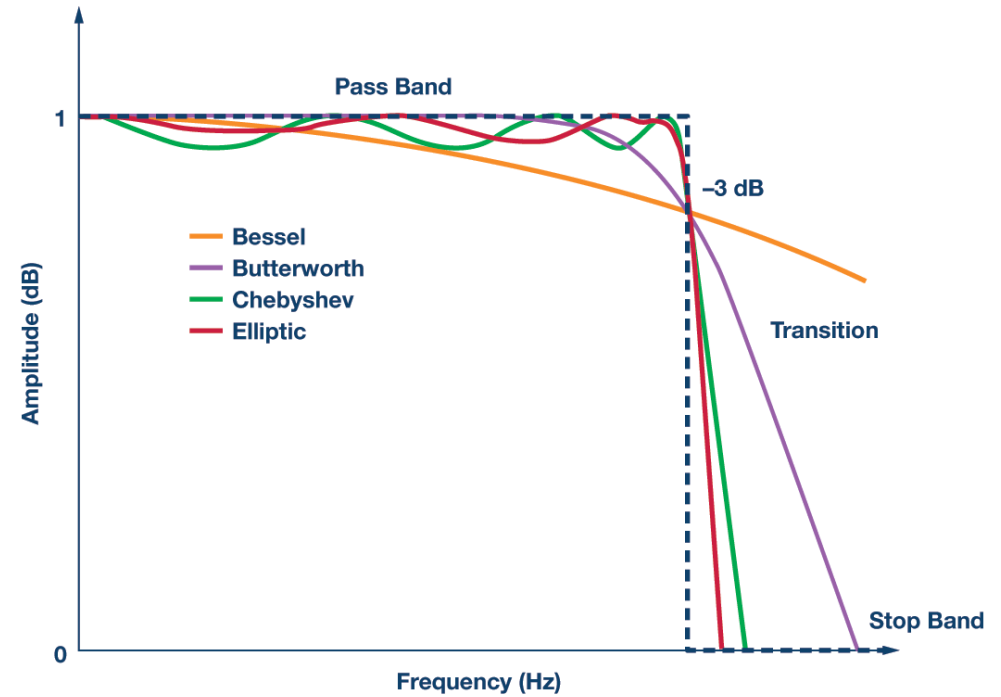

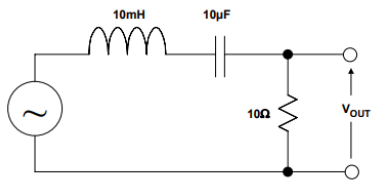
$$H(s) = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0} \quad s = j\omega$$



$$\rightarrow H(s) = \frac{V_o}{V_{in}} = \frac{RCs}{LCs^2 + RCs + 1}$$

Measuring filters: S-parameters of a 4-poles

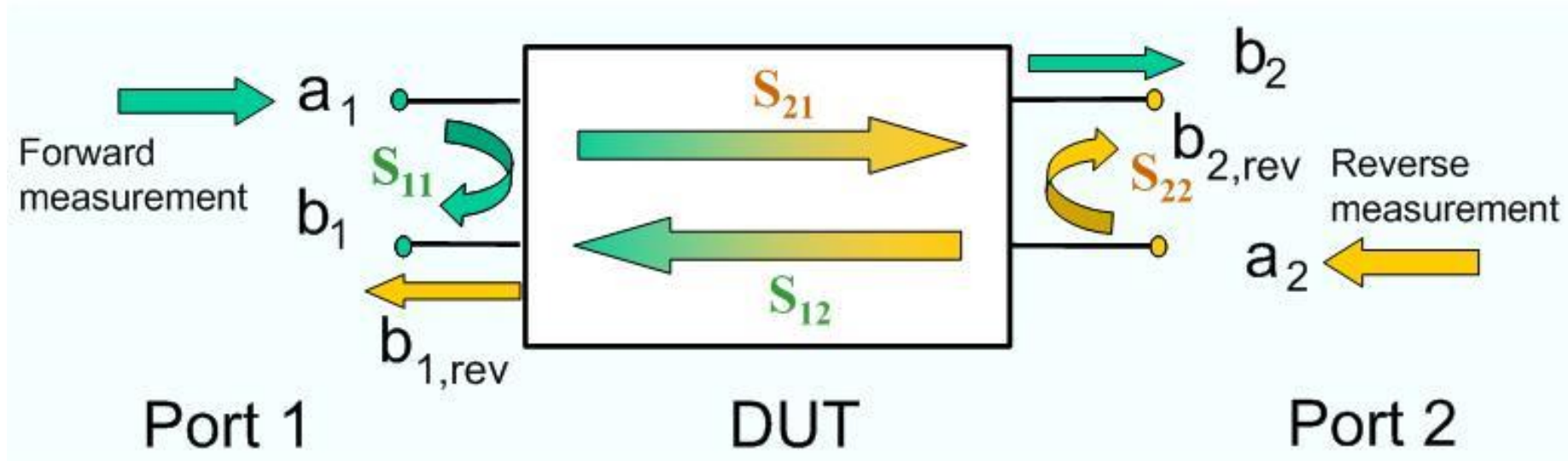S-parameters are the basic measured quantities of a network analyzer. They describe how the DUT modifies a signal that is transmitted or reflected in forward or reverse direction. For a 2-port measurement the signal flow is as follows.



- S11** is the input port voltage reflection coefficient
- S12** is the reverse voltage gain
- S21** is the forward voltage gain
- S22** is the output port voltage reflection coefficient

Measuring filters: S-parameters and VSWR

Return Loss can be thought of as a measure of how close the actual input/output impedance of the network is to the nominal system impedance value.

$$RL_{in} = 10 \log_{10} \left| \frac{1}{S_{11}^2} \right| = -20 \log_{10} |S_{11}| \text{ dB}$$

$$RL_{out} = -20 \log_{10} |S_{22}| \text{ dB}$$

VSWR is defined as $VSWR = \frac{1 + |S_{11}|}{1 - |S_{11}|}$

$$\Gamma = \frac{ZL - Z0}{ZL + Z0}$$


$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$VSWR = \frac{Vmax}{Vmin}$$




satoms.com

VSWR and Reflected Power (%)

VSWR	% of Reflected Power
1.0	0
1.5	4
2.0	11.1
3.0	25
4.0	36
5.0	44
6.0	51
7.0	56.3
8.0	60.5
9.0	64
10	66.9
15	76.6
20	81.9
satoms.com	

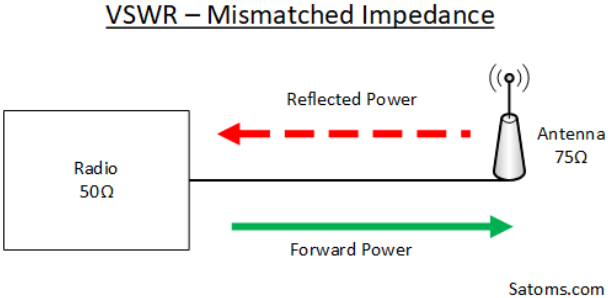


Measuring filters: S-parameters and VSWR

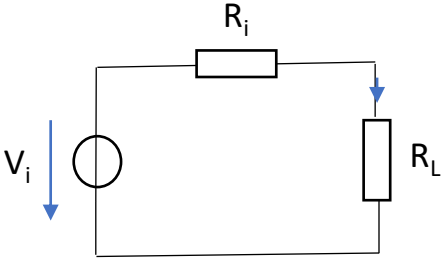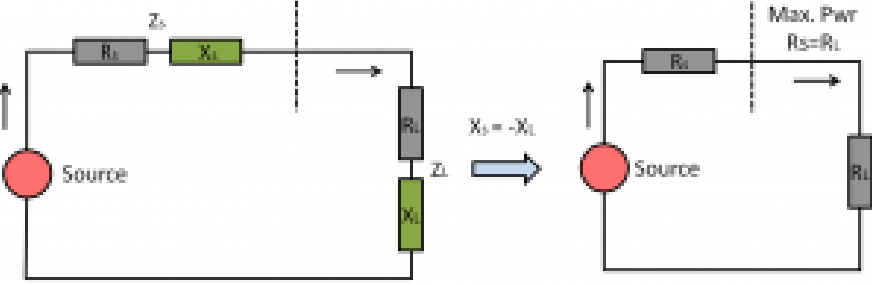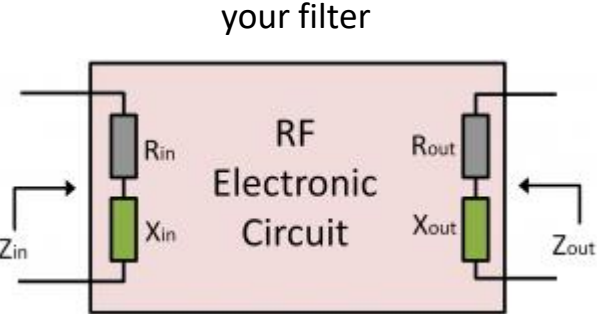

$$P_L = \left(\frac{V_i}{R_i + R_L}\right)^2 * R_L$$

max. power transfer @R_i = 50 Ohm

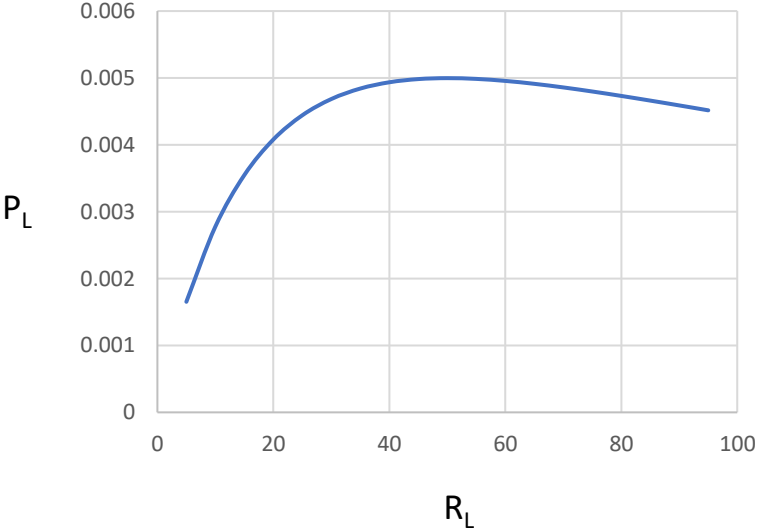

Nano VNA

- Frequency: 50kHz-3GHz
- RF output power: -9dBm (error within 1GHz: ± 1 dB)
- Frequency accuracy: <0.5 ppm
- S21 dynamic ranges: 70dB (1.5GHz), 60dB (3GHz)
- S11 dynamic ranges: 50dB (1.5GHz), 40dB (3GHz)
- 2-port return loss: 20dB typ (1.5GHz), 13dB min (3GHz)
- Number of calibration points: 101 points
- Number of scanning points: 101 points
- Number of traces: 4
- Number of mark points: 4 (the mark point bar can be moved up and down on the screen)
- USB interface: USB Type-C communication mode: CDC (serial)



Analog Devices: <https://www.youtube.com/watch?v=j0K4yboux7g>